



Description:

The circuit overleaf implements a 4-bit version of the Register-file section of the datapath shown in Mano and Kime figure 7-9 (or 4th lecture, page 12), by using components designed in VHDL.

1. Design the VHDL components (Register, Decoder, and two Multiplexer 32 bit) and interconnect them to build a register-file. The schematic shows only four registers. Your solution should implement 32 registers.
2. You should provide test benches and simulations that prove the correctness of the following operations:
 - a. Load your StudentID (HEX value) into the first of the 32 registers. Then load your StudentID - 1 (HEX value) into the 2nd register, your StudentID - 2 (HEX value) into the 3rd register... Please continue until all 32 registers have a value.
 - b. Transfer the contents of any register to any other register, i.e. that it can execute the transfers $R_i \leftarrow R_j$, $i, j = 0, 31$ (show 10 examples)



